



VERIFICATION OF A 65NM CMOS IC FOR VARIOUS APPLICATIONS (NEUTRINO DETECTION, HIGH ENERGY PHYSICS, ETC.)

18TH APRIL 2018 | CHRISTIAN ROTH

VULCAN CHIP OVERVIEW

• The Vulcan Chip

- **Highly linear**, fully integrated circuit – **Vulcan**


- Sampling ADC with approx. **80 dB linearity**
(3 signal chains with 3 different gains)
- No external components required
- On-chip clock generation from ref. clock

- Precise signal reconstruction


- No analog delay line
(reducing noise & distortion)
- Control loop to suppress DC variations
- Optional overshoot compensation

- Further key parameters of Vulcan:

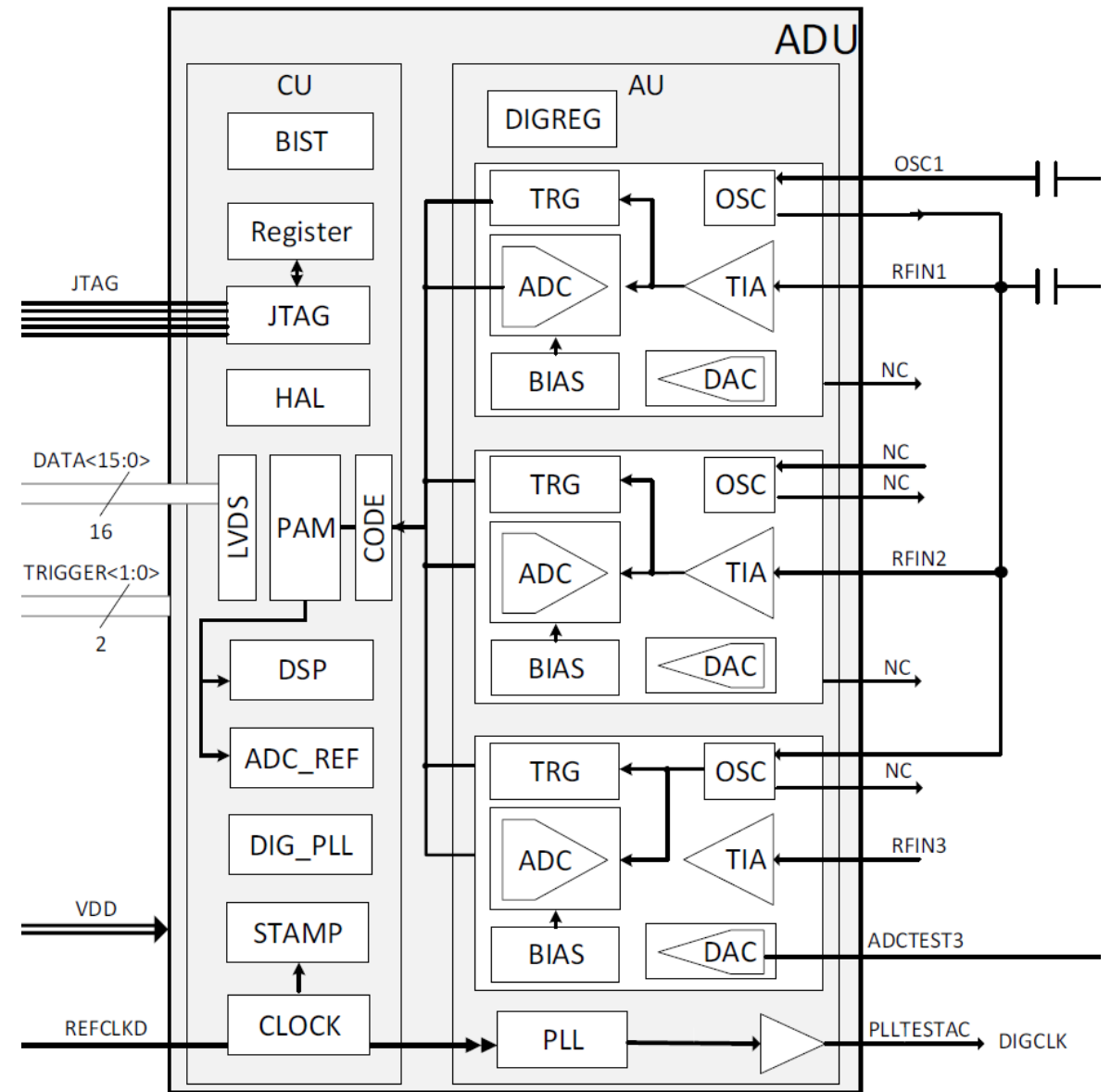- ADC with **9.5 bit** (3x 8 bit), **1 Gsample/s**
- Transimpedance Amplifier (TIA)
Input impedance of **< 10 Ohm**
- Power consumption ~ **1.2 Watt**




VULCAN IC LAYOUT

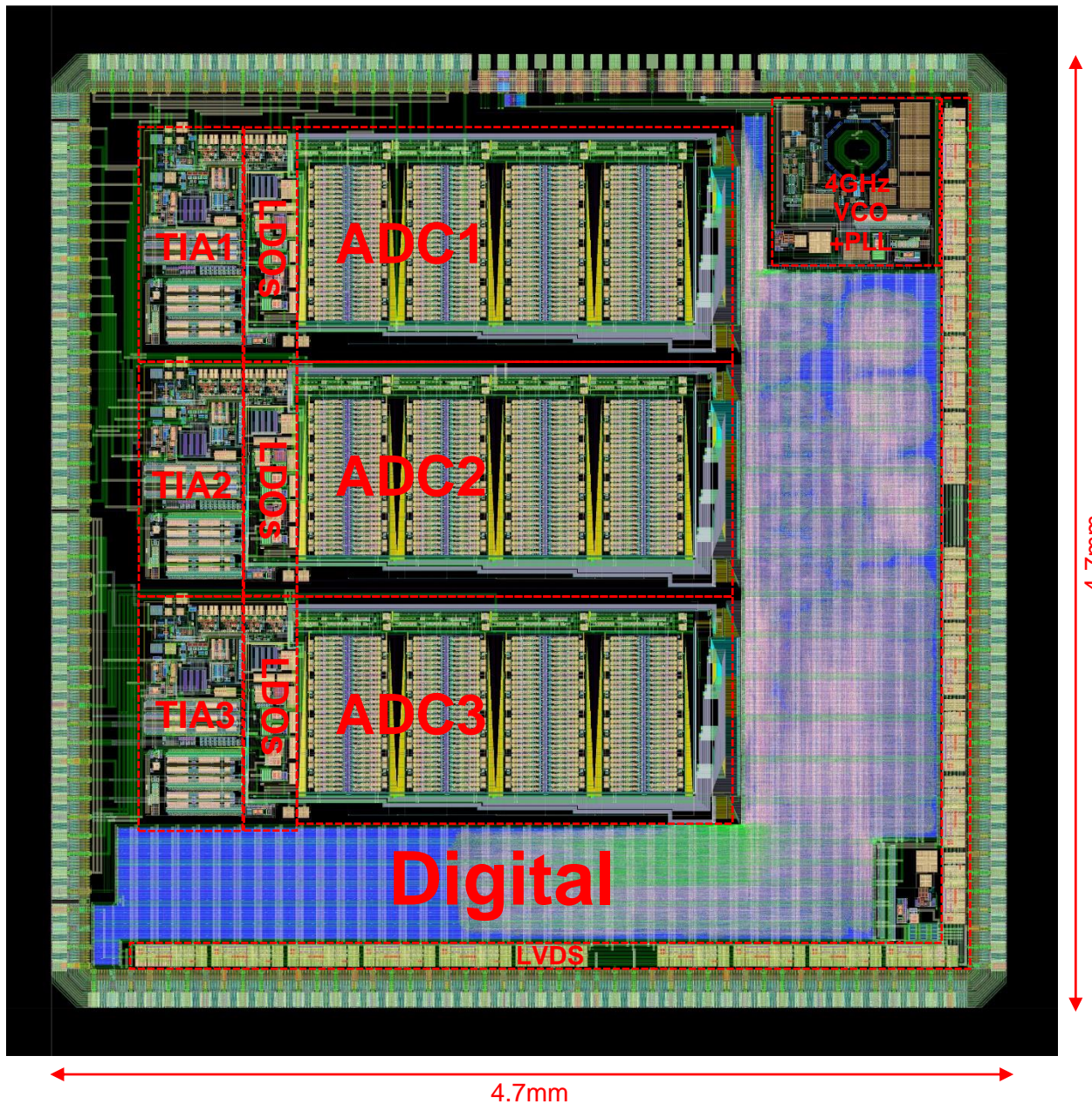

Key Parameter of Vulcan	
Process	65 nm CMOS
Active Area	22 mm ²
Power	~ 1.2 W
Input Impedance	< 10 Ohm
Input Bandwidth	500 MHz
Sampling Rate	1 Gsample/s
Dynamic Range	80 dB
ADC Resolution	3x 8 bit
High Gain	0.06 p.e./bit
Medium Gain	0.4 p.e./bit
Low Gain	8 p.e./bit


VULCAN SIGNAL MODES

- Signal Modes – Small & Medium Signals

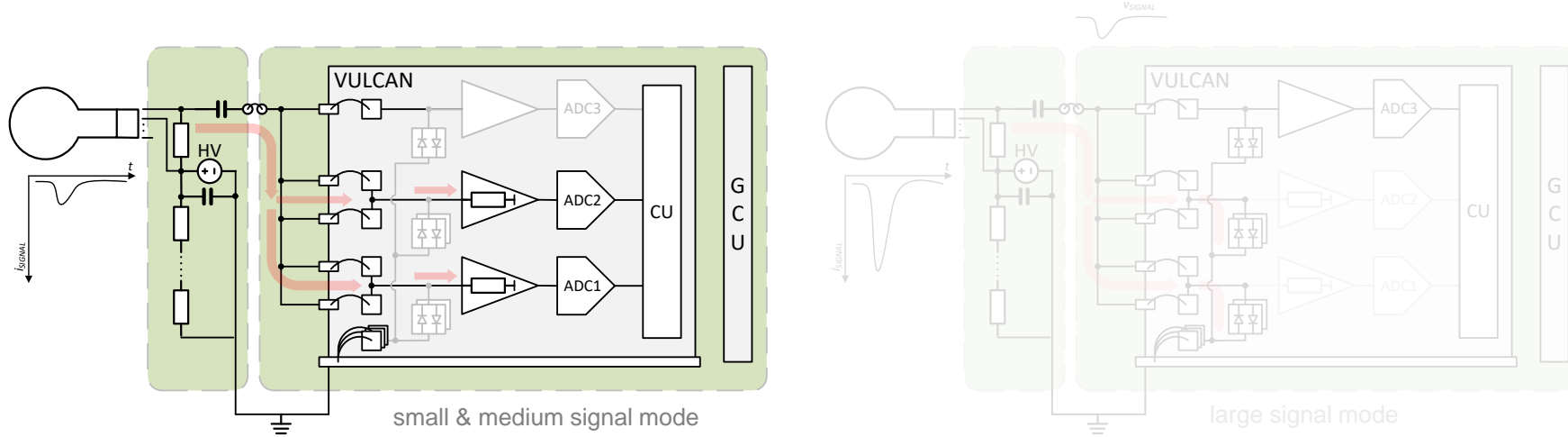

First two signal chains

 
- Parallel TIA input
- Programmable gains
- Combined input resistance $R \approx 5 \Omega$



patent pending


VULCAN SIGNAL MODES

- Signal Modes – Large Signals

 


Third signal chain

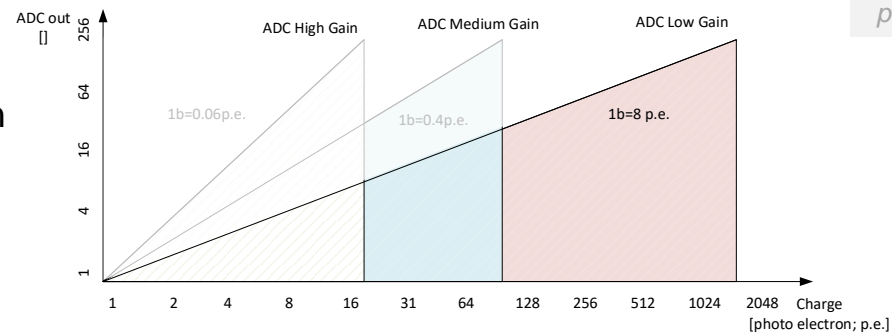- Current $> 20 \text{ mA}$
- TIA input saturates, ESD diodes open
- Voltage over diodes measured
- Combined input resistance $R \approx 5 \Omega$




LAB SETUP OVERVIEW

 

BOARD CONCEPT


Verification Board

 - Board for IC Verification
- Every ADC can be measured
- Best RF/Impedance performance
- Optimized for verification measurements




Socket Board

 - Socket can be populated on board
- For measurement of many samples
- Limited performance measurements
- Functional checks





PMT Board

 - For direct usage with PMT
- Protection circuit
- All 3 ADCs connected




System Board

  - All 3 ADCs connected
- Protection circuit
- Reference design for system implementation




Main Board

 
- Logic analyser connection
- Power supply connection
- JTAG interface
- DC measurements
- Samtec board to board connectors





VERIFICATION BOARD CONCEPT

 


VERIFICATION BOARD

 

VERIFICATION BOARD


 
 


VERIFICATION BOARD SETUP

 


SOCKET BOARD SETUP

- Yamaichi Socket for functional testing

   


VERIFICATION SOFTWARE FRAMEWORK


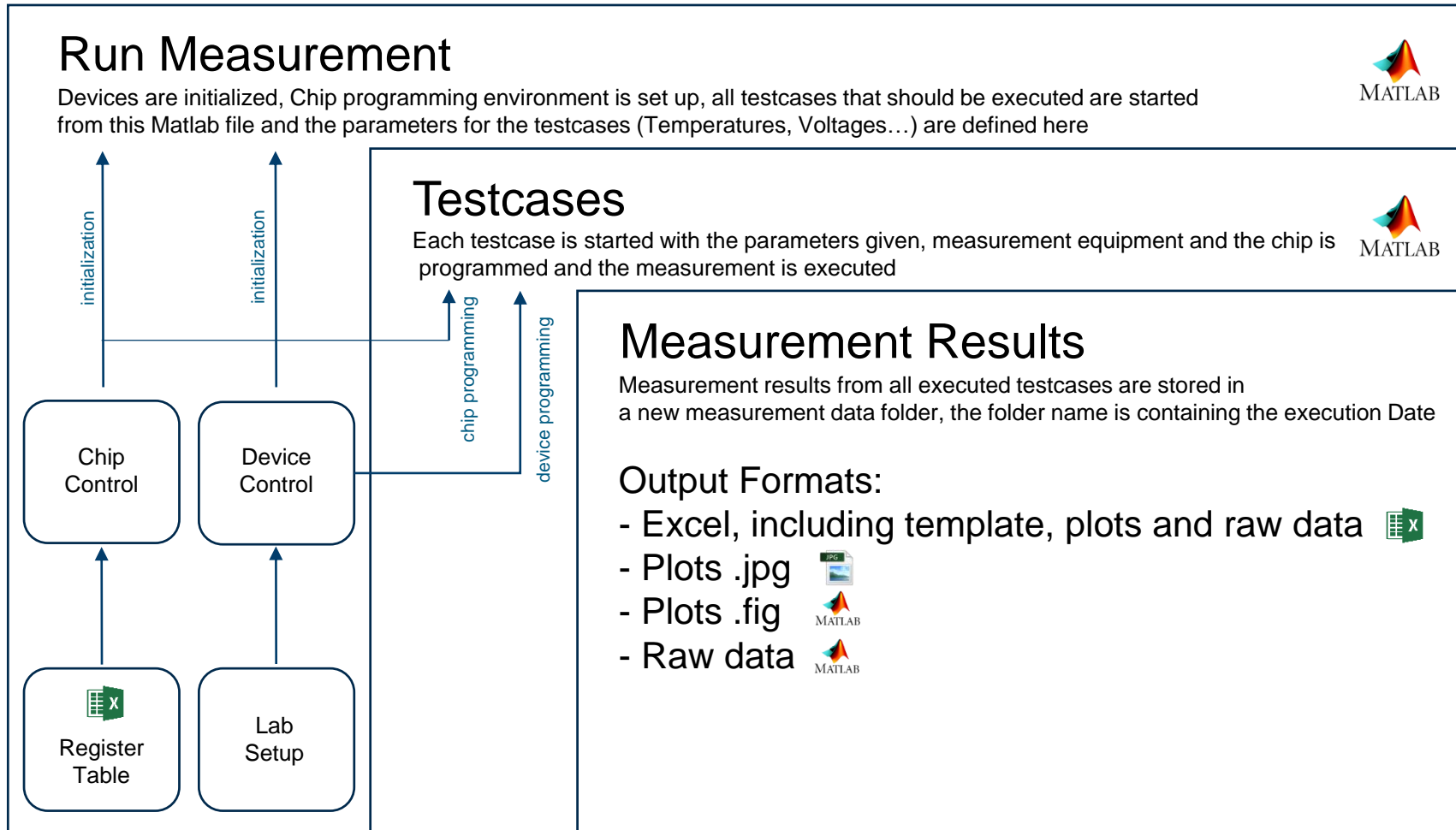


VERIFICATION RESULTS OF VULCAN ES2

- LVDS Data Lines

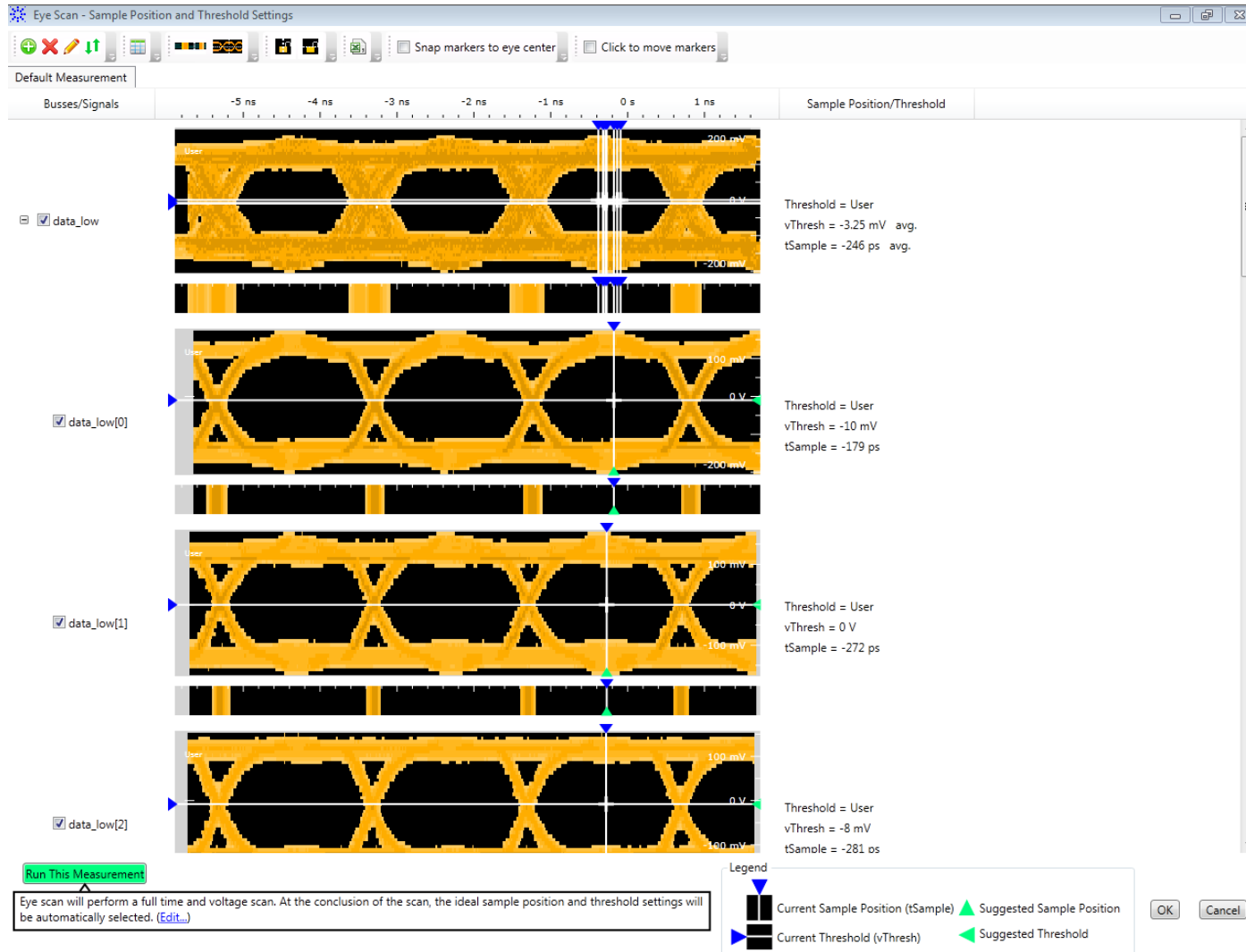

VCO AND PLL INVESTIGATIONS

  

Date: 15.DEC.2003 07:15:24


- VCO running @4GHz
- Reference clock for PLL @31.25MHz
- Measurement VCO/4 -> 1GHz

Date: 15.DEC.2003 07:17:58





CLOCK AND PLL INVESTIGATIONS

- VCO Tuning Range @ 25°C

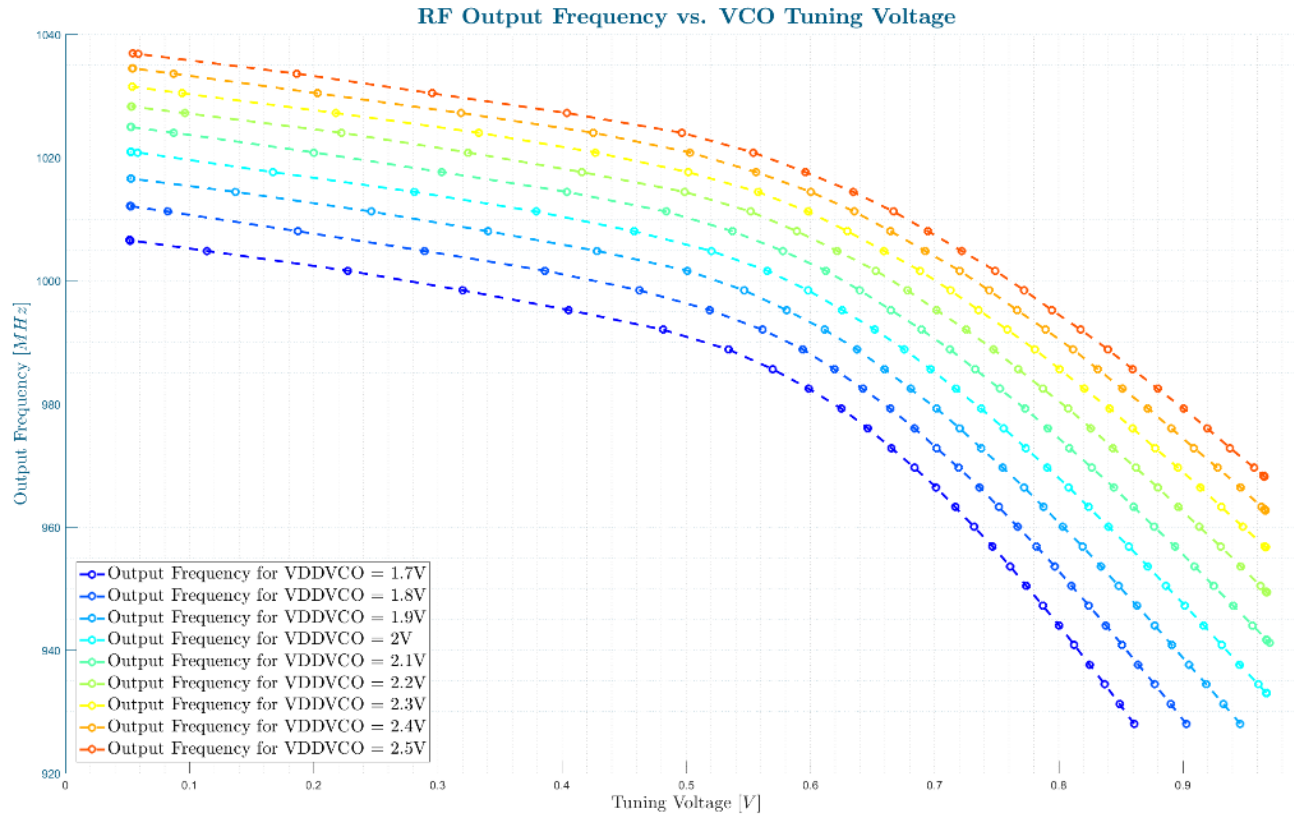


- PLL Phase Noise @ 25°C

 

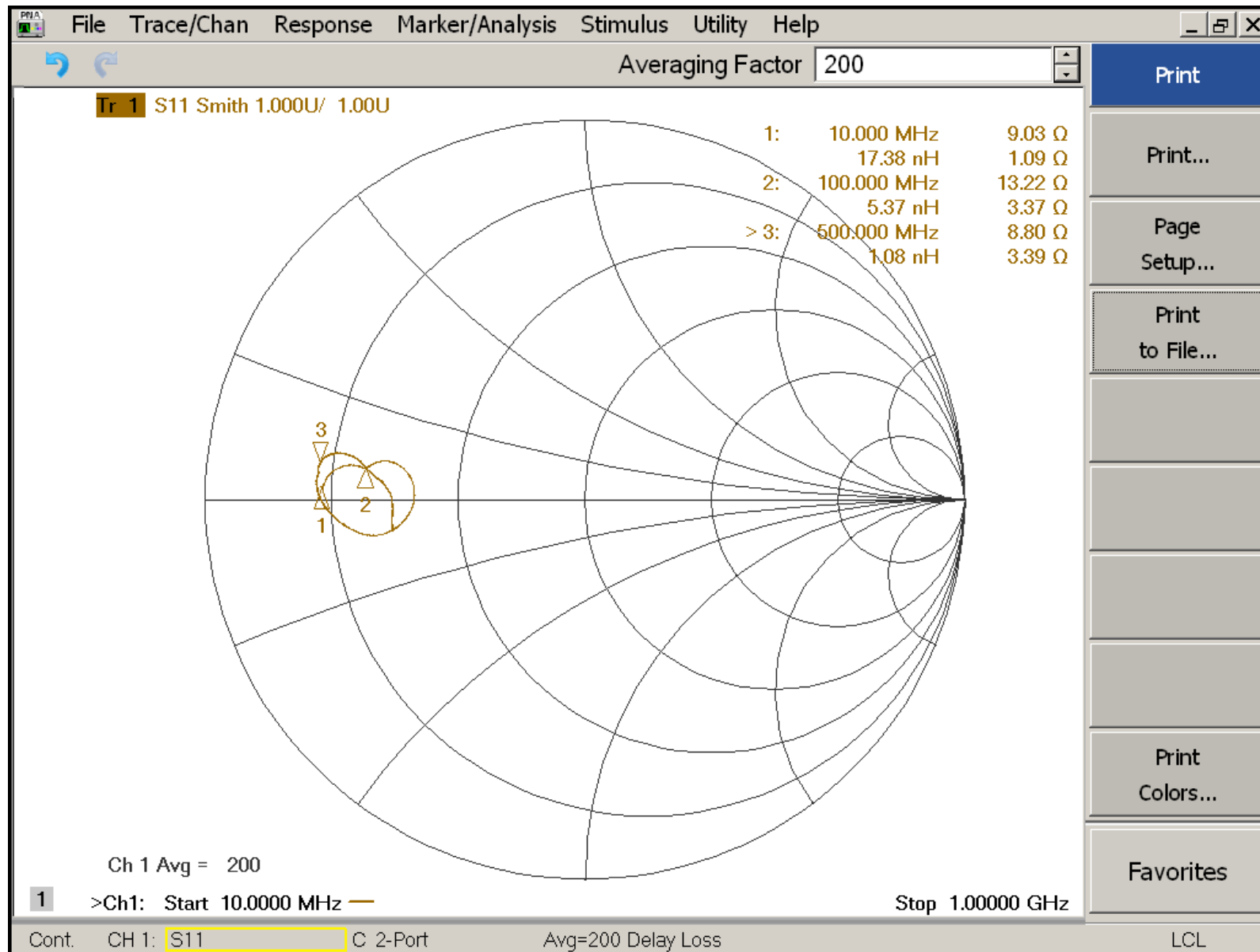



TRANSIMPEDANCE AMPLIFIER INPUT IMPEDANCE

TIA Low Gain

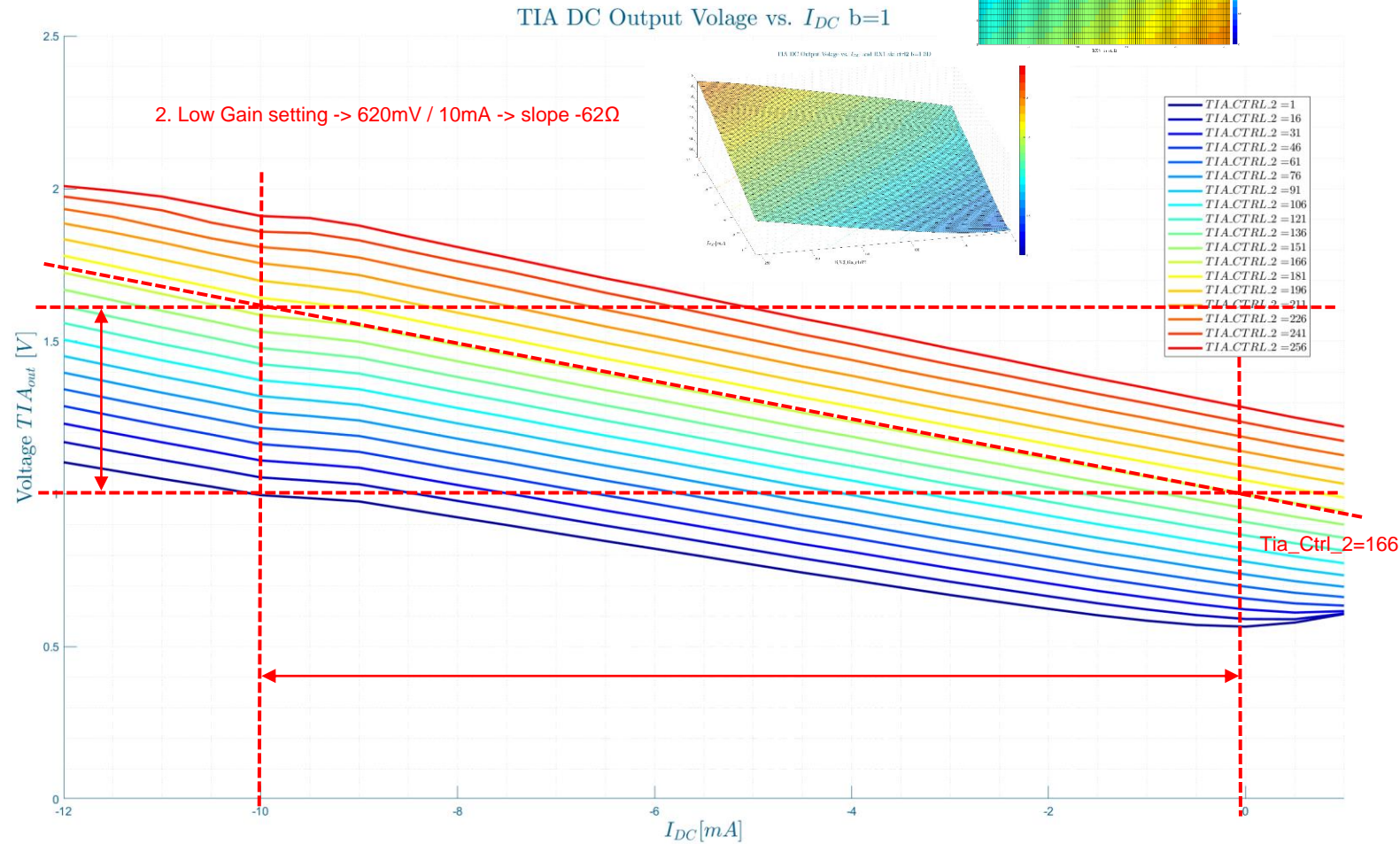

TIA High Gain

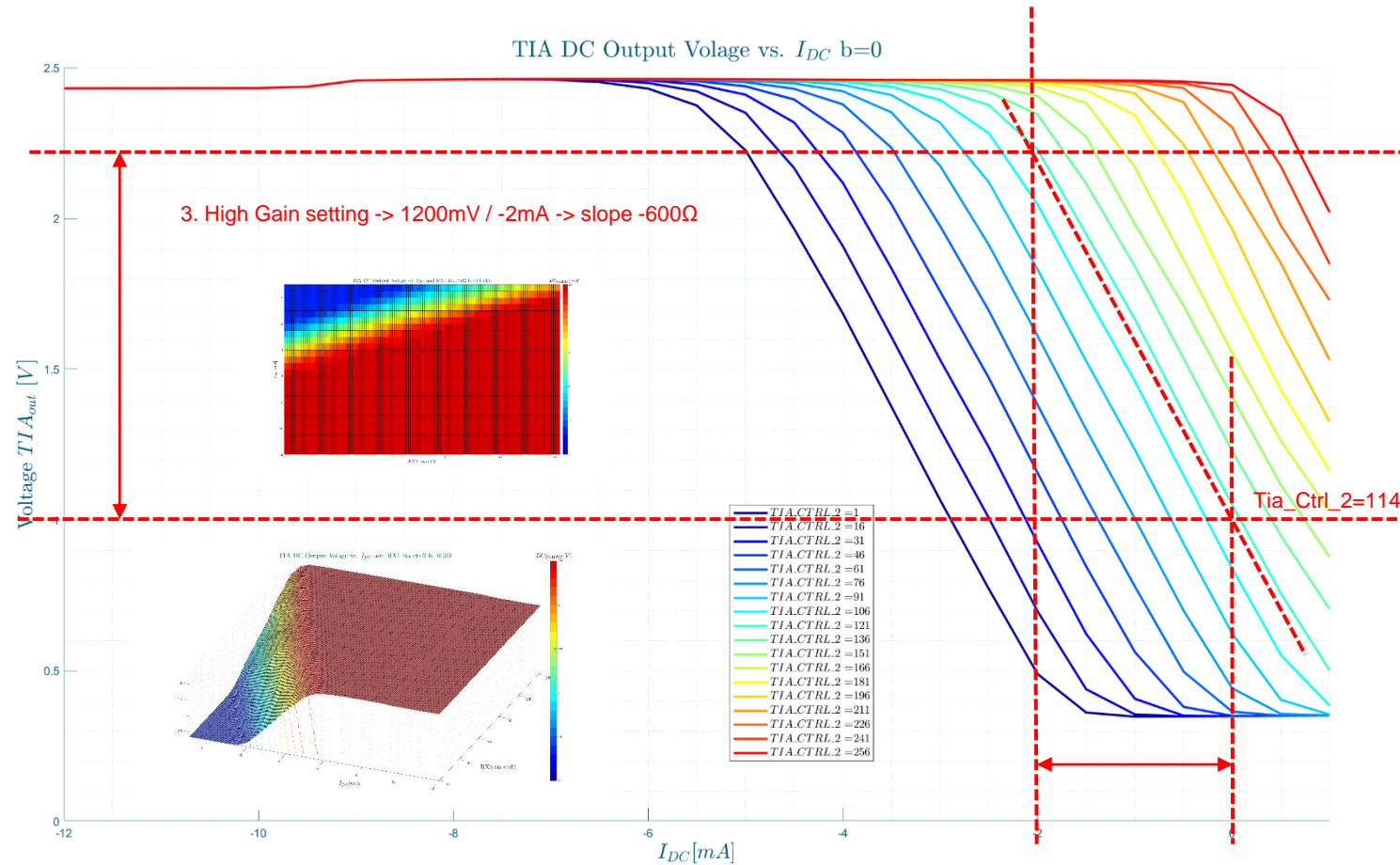


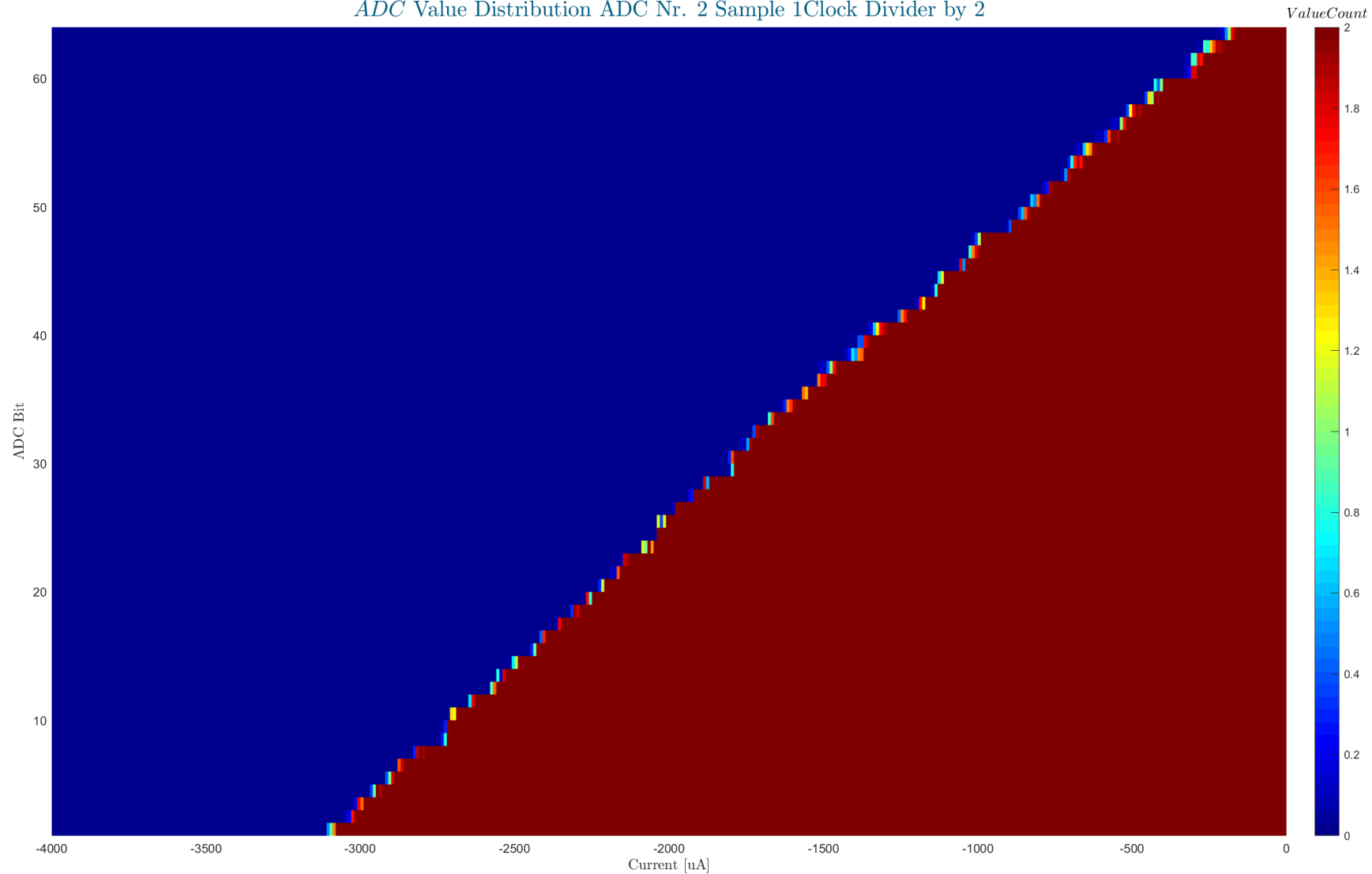


ADC Thermometer Code Distribution 500Msample/s

Full Range ADC Characteristic (low Gain)

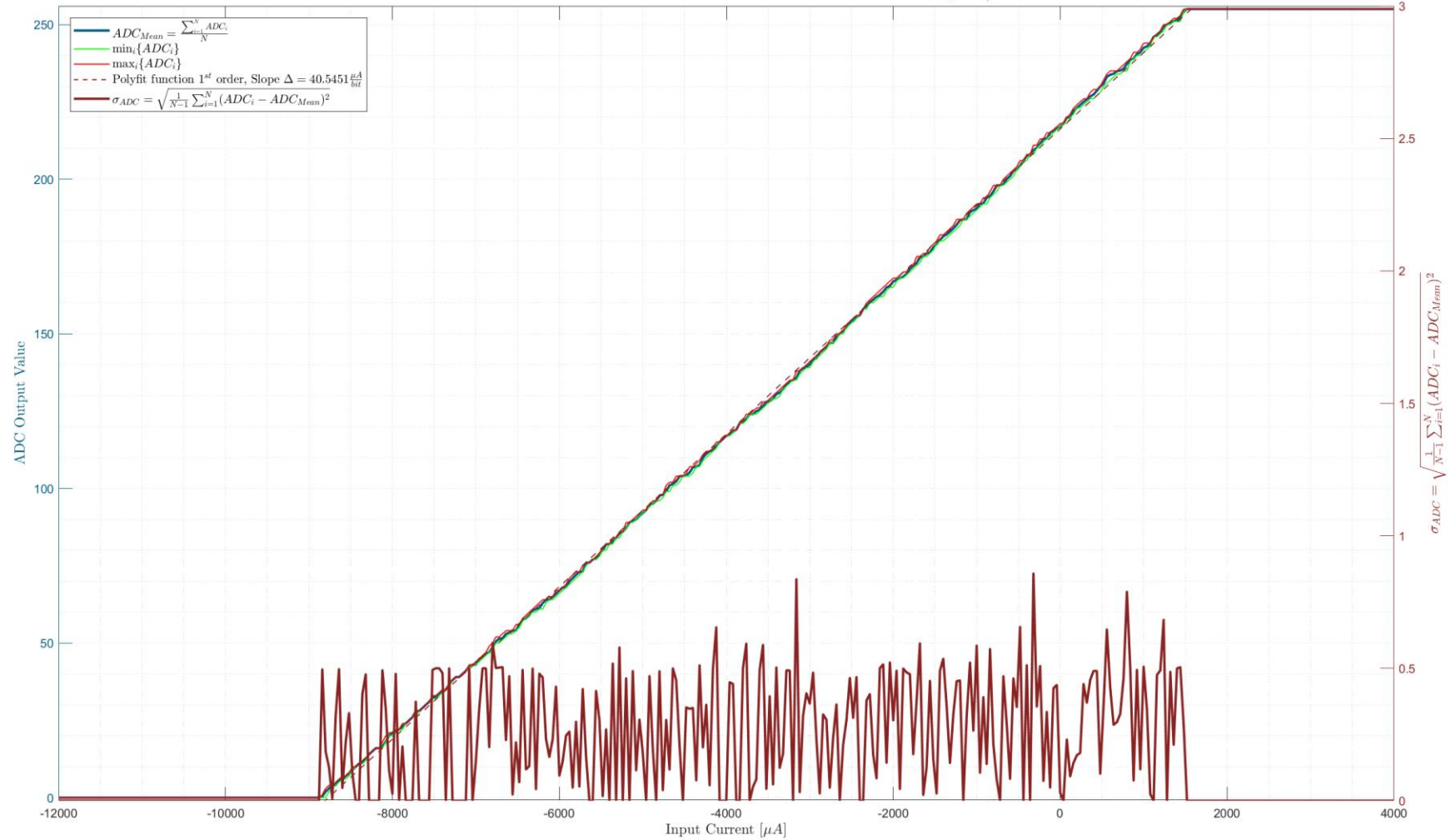
Vulcan 2.0 RX1 ADC Measurement 700M Samples/s




Full Range ADC DNL (low Gain)

 


Full Range ADC INL (low Gain)

 


Sinewave Signal 1 MHz (700Msamples/s)

 



SNR Measurement (700Msamples/s)

 

 SNR Measurement with Distortion (700MSamples/s)



10ns Pulse ADC Output

  

Vielen Dank!

